

## A Digitally Programmable Gain and Attenuation Amplifier Design

by James Wong

By adding two resistors to the output amplifier feedback loop of a current output D/A converter, you can get gain control in addition to attenuation control. Figure 1 shows a complete digitally programmable amplifier that is capable of producing gain as well as attenuation in the range of 1/64 to 64. The circuit derives its range by using a 12-bit CMOS D/A converter.


The design is based on the fact that the transfer function from the input to the output of the D/A converter is purely voltage attenuation. Connecting the two resistors  $R_1$  and  $R_2$  in a "T" configuration inside the feedback loop of the output amplifier produces a voltage gain from the resistor junction to the output. If  $R_1$  is much smaller than  $R_{FB}$  (in this case  $R_{FB}$  is 11k $\Omega$ ), then the gain produced is approximately equal to  $1 + R_2/R_1$ , or 64. The result is a programmable gain amplifier that has a transfer function of:

$$A_v = -\left(\frac{D}{4096}\right)(64),$$


where D represents the binary weighted digital code of the D/A converter.

Of course, the added gain of the T-network does increase the noise gain of the circuit. Be sure to choose a low noise amplifier to begin with.

By using a low noise, high-frequency op amp such as the OP-61, besides keeping noise level down, it gives the circuit a wide bandwidth performance even at high-gain settings.

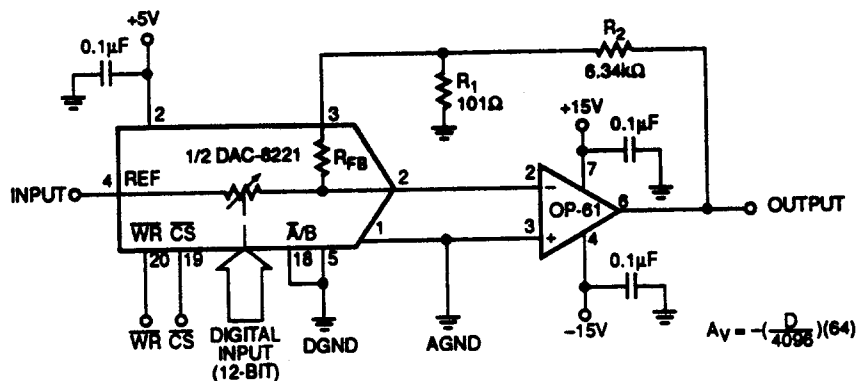

**FIGURE 1:** Two Resistors  $R_1$  and  $R_2$  Add a Gain of 64 to the D/A Converter, Resulting in a Simple Digitally Programmable Gain Amplifier

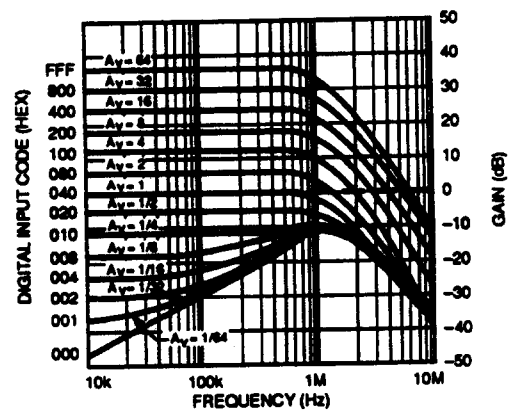

**FIGURE 2:** Gain vs. Frequency Response for the Twelve Binary Gain Settings

Figure 2 shows the frequency response of the programmable gain circuit at various gain settings. At high gains, the amplifier has 1MHz bandwidth. At gains below 1/4, the D/A converter's stray capacitance feedthrough limits the amplifier bandwidth, while still achieving 20kHz.