

65V, 500mA Step-Down Converter Fits Easily into Automotive and Industrial Applications

Design Note 512

Charlie Zhao

Introduction

The trend in automobiles and industrial systems is to replace mechanical functions with electronics, thus multiplying the number of microcontrollers, signal processors, sensors and other electronic devices throughout. The issue is that 24V truck electrical systems and industrial equipment use relatively high voltages for motors and solenoids while the microcontrollers and other electronics require much lower voltages. As a result, there is a clear need for compact, high efficiency step-down converters that can produce very low voltages from the high input voltages.

65V Input, 500mA DC/DC Converter with an Adjustable Output Down to 800mV

The LTC[®]3630 is a versatile Burst Mode[®] synchronous step-down DC/DC converter that includes three pinselectable preset output voltages. Alternatively, the output can be set via feedback resistors down to 800mV. An adjustable output or input current limit from 50mA to 500mA can be set via a single resistor. The hysteretic nature of this topology provides inherent short-circuit protection. Higher output currents are possible by paralleling multiple LTC3630s together and connecting the FBO of the master device to the VFB pin of a slave device. An adjustable soft-start is included. A precision RUN pin threshold voltage can be used for an undervoltage lockout function.

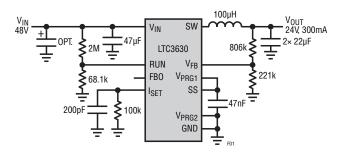


Figure 1. High Efficiency 24V Regulator with Undervoltage Lockout and 300mA Current Limit

24V Regulator with 300mA Output Current Limit and Input Undervoltage Lockout

Figure 1 shows a 48V to 24V application that showcases several of the LTC3630's features, including the undervoltage lockout and output current limit. Operational efficiencies are shown in Figure 2.


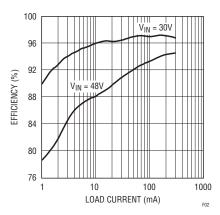


Figure 2. Efficiency of Circuit in Figure 1

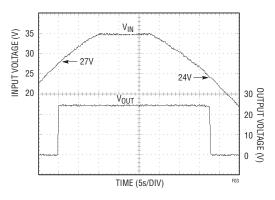



∠7, LT, LTC, LTM, Linear Technology, the Linear logo and Burst Mode are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

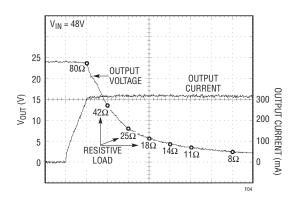


Figure 4. Resistive Load Sweep vs Output Current vs Output Voltage with Output Current Limit Set to 300mA

The RUN pin is programmed for V_{IN} undervoltage lockout threshold levels of 27V rising and 24V falling. Figure 3 shows V_{OUT} vs V_{IN}. This feature assures that V_{OUT} is in regulation only when sufficient input voltage is available.

The 24V output voltage can be programmed using the 800mV 1% reference or one of the preset voltages. This circuit uses the 5V preset option along with feedback resistors to program the output voltage. This increases circuit noise immunity and allows lower value feedback resistors to be used.

Although the LTC3630 can supply up to 500mA of output current, the circuit in Figure 1 is programmed for a maximum of 300mA. An internally generated 5µA bias out of the I_{SET} pin produces a voltage across an I_{SET} resistor, which determines the maximum output current. Figure 4 shows the output voltage as a resistive load is varied from approximately 100 Ω down to 8 Ω while maintaining the output current near the programmed value of 300mA. In addition, the hysteretic topology used in this DC/DC converter provides inherent short-circuit protection.

Input Current Limit

Another useful feature of the LTC3630 is shown in Figure 5. In this 5V circuit, the current limit is set by a resistive divider from V_{IN} to I_{SET} , which produces a voltage on the I_{SET} pin that tracks V_{IN} . This allows V_{IN} to control output current which determines input current.

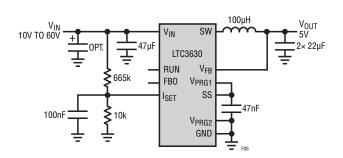


Figure 5. 5V Regulator with 55mA Input Current Limit

An increased voltage on I_{SET} increases the converter's current limit. Figure 6 shows the steady-state input current vs input voltage and the available output current before the output voltage begins to drop out of regulation. For the values shown in Figure 5, the input current is limited to approximately 55mA over a 10V to 60V input voltage range.

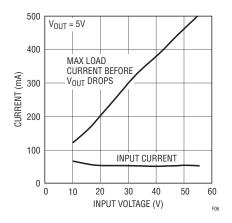


Figure 6. Input Voltage vs Load Current and Input Current with Input Current Limit Circuit Shown in Figure 5

Conclusion

The LTC3630 offers a mixture of features useful in high efficiency, high voltage applications. Its wide output voltage range, adjustable current capabilities and inherent short-circuit tolerant operation makes this DC/DC converter an easy fit in demanding applications.

Data Sheet Download

www.linear.com/3630

Linear Technology Corporation 1630 McCarthy Blvd., Milpitas, CA 95035-7417 (408) 432-1900 • FAX: (408) 434-0507 • www.linear.com For applications help, call (408) 432-1900, Ext. 3258

dn512 LT/AP 0313 196K • PRINTED IN THE USA