

## Low Power Op Amp: Low Power Filter, Headphone Driver Revisited

Design Note 563

by Aaron Schultz

## Introduction

A new family of op amps features industry leading speed versus supply current. The LTC6261/LTC6262/ LTC6263 family (single, dual, quad) provides 30MHz at a low 240µA supply current, with 400µV maximum offset voltage and rail-to-rail input and output. In combination with 1.8V to 5.25V supply, these op amps enable applications requiring uncompromised performance with low power and low voltage.

## Bridge-Tied Differential Output Amplifier

The low supply current at the bandwidth and noise performance allows for excellent fidelity at a fraction of the usual dissipation in portable audio equipment. As with active filters, revisiting portable audio equipment headphone drivers is a rational enterprise, given the unique capabilities of the LTC6261.

Headphone speaker impedances range from  $32\Omega$  to  $300\Omega$ ; their responsivity, from 80dB to 100dBSPL per 1mW and beyond. As an example, considering a headphone speaker with 90dBSPL per 1mW, it takes

100mW delivered to reach 110dBSPL. With  $32\Omega$ , the RMS current is 56mA and voltage 1.8V; with  $120\Omega$ , 29mA and 3.5V.

Given a 3.3V supply and the output of one LTC6261 amplifier, there may not be sufficient drive capability to yield 100mW. However, the combination of two 180° phased amplifiers is enough to provide the necessary drive to reach upwards of 100mW delivered power. Duplication of this bridge drive circuit enables power to both left and right sides.

The LTC6263 provides four amplifiers in one small package. Data from a 2-amplifier LTC6262 driving what could be left or right is shown in Figures 2 and 3. Basic current consumption of the two amplifiers, with as much as  $1V_{P-P}$  input but no load, is 500µA.

The circuit consists of first, an inverting gain stage with closed loop gain = 1.5, and a subsequent inverting stage. The combination of inverting stages produces a single-ended input to differential output gain of 3.

 ${\boldsymbol {\cal T}}$ , LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Analog Devices, Inc. All other trademarks are the property of their respective owners.



Figure 1. Audio Headphones Bridge Driver





Figure 2. LTC6262 Bridge Driver THD and Noise with Different Loads vs Frequency

With 500mV<sub>P-P</sub> input, the output is 1.5V<sub>P-P</sub>, or 0.75V max, or 0.53V<sub>RMS</sub>. With 50 $\Omega$ , 500mV input leads to approximately 5.6mW delivered power. At 1V<sub>P-P</sub> input, the circuit delivers 22.5mW. Note that it helps that the LTC6261 output can swing close to rail-to-rail with load.

The first build of this circuit in the lab produced a significant tone at a few hundred Hz. It turned out that the positive input was not well grounded as an "AC ground" over all frequencies because the voltage was not strongly pegged. The need to peg the voltage arises when using a single supply rather than a dual supply. With a single supply,  $V_M$  is not ground, but rather a mid-rail voltage created to enable inverting topologies to work properly. The resistor divider that creates  $V_M$  has large resistance values (for example, two 470k in series) to minimize additional supply current. A large capacitor ensures a strong ground at low frequencies. Indeed, the addition of a large capacitor (1µF, which forms a pole with the 470k resistors in parallel) eliminated the mysterious distortion tone.



Figure 3. LTC6262 Bridge Driver THD and Noise with Different Loads vs Amplitude at 1kHz

Despite the low quiescent current, this driver delivers low distortion to a headphone load. At high enough amplitude, distortion increases dramatically as the op amp output clips. Clipping occurs sooner with more loading as the output transistors start to run out of current gain.

One significant concern in a portable device is battery drain. Music played loudly, or listeners' musical choices affect the rate of battery drain. The end-use of a device is out of the designer's control. Quiescent current, though, is not. Because much of a device's time may be spentidle, quiescent current is significant, as it drains batteries continuously. The LTC6261's low quiescent current increases battery discharge time.

## Conclusion

The applications shown here take advantage of a unique combination of features available in the LTC6261 op amp family. The low quiescent current of these devices does not diminish their ability to perform at levels usually reserved for more power hungry parts. Rail-to-rail input and output, shutdown, and choice of package are features that add to their versatility.

Data Sheet Download

www.linear.com/LTC6261

DN563 LT/TP 0617 71K • PRINTED IN THE USA © LINEAR TECHNOLOGY CORPORATION 2017 For applications help, call (408) 432-1900, Ext. 3409

