


Edited by Bill Travis

## Fleapower flasher draws less than 50 $\mu\text{A}$

Gary Butterfield, IEC Electronics Technology Center, Newark, NY

**S**OME APPLICATIONS REQUIRE a circuit to indicate that a battery's voltage has fallen below a certain value. However, if you don't frequently check the indicator, the low-battery indicator itself can easily discharge the battery. The circuit in **Figure 1** indicates when the battery voltage has dropped below a preset value. The circuit draws less than 50  $\mu\text{A}$ , regardless of whether the indicator flashes. IC<sub>1A</sub> operates as a simple comparator. IC<sub>1A</sub>'s Pin 2 provides the reference voltage to Pin 2 of comparator IC<sub>1A</sub>. Resistor R<sub>1</sub> provides an adjustable trip point. A potentiometer setting of 124 k $\Omega$  yields a trip point of approximately 10.3V. When the power-supply voltage is above the trip point, IC<sub>1A</sub>'s Pin 1 is high, forward-biasing diode D<sub>1</sub> and holding the flasher in the off state. R<sub>2</sub> provides approximately 300 mV of hysteresis for the detector. IC<sub>1B</sub> provides the flashing of the LED. C<sub>1</sub> charges through R<sub>3</sub>, and, when its voltage exceeds the voltage at IC<sub>1B</sub>'s Pin 5, Pin 7 pulls low, discharging the capacitor through the LED. Resistors R<sub>4</sub> and R<sub>5</sub> provide a voltage reference, and resistor R<sub>6</sub> provides hystere-

**Figure 1**

 

**This fleapower flasher indicates a low-battery condition with a flashing LED.**

sis of approximately one-third of the supply voltage.

The circuit's current consumption is 45  $\mu\text{A}$  at 10V, climbing to 48  $\mu\text{A}$  at 12V. The state of the flasher does not affect current consumption, because the LED receives its power via the capacitor. You have to make a number of trade-offs to achieve this low current consumption:

For example, discharging the capacitor through the LED allows the circuit to reuse the capacitor's charge, instead of dumping it to ground. It also eliminates the current spikes that occur when driving the LED from the supply rail. However, the charge on the capacitor limits the resulting LED brightness, so you should use high-efficiency LEDs when possible.

Another trade-off is that the LED affects the minimum operating voltage because of the forward voltage drop of the diode. In the prototype, a red LED works down to a lower operating voltage of 4.3V. A yellow LED in the same circuit operates down to 6.4V. Additionally, the high resistances on the board, most notably the resistors attached to IC<sub>1B</sub>'s Pin 5, require careful attention to board cleanliness. Small leakage currents can significantly affect circuit operation and current drain. You can reduce the values of these resistances to improve manufacturability at the expense of higher current consumption.

**Is this the best Design Idea in this issue?** Select at [www.edn.com](http://www.edn.com).


Fleapower flasher draws less than 50 $\mu\text{A}$ .....	<b>75</b>
PC-based configurable filter uses no digital potentiometers .....	<b>76</b>
Frequency source feeds entire lab .....	<b>80</b>
Circuit sequences supplies for FPGAs .....	<b>82</b>

**Publish your Design Idea in EDN. See the What's Up section at [www.edn.com](http://www.edn.com).**

# PC-based configurable filter uses no digital potentiometers

Saurav Gupta and Tejinder Singh, New Delhi, India


**M**ODERN INSTRUMENTATION requires digital control signals. These signals come from a central microprocessor or, in modern context, the popular parallel or serial PC ports. In recent times, digital potentiometers have eliminated the hassles from this interface for the analog section. Designers can replace the resistors of the analog design with digital potentiometers, thus providing the necessary digital control. However, digital potentiometers suffer more severely from temperature-sensitive performance drifts than their manual counterparts, and they exhibit finite wiper-resistance effects. The design in **Figure 1** represents a multifunction, analog biquadrature design for automated mixed instrumentation. You can configure the design for both Q factor and center frequency via a PC's parallel port. The circuit requires no DACs or digital potentiometers. The circuit,

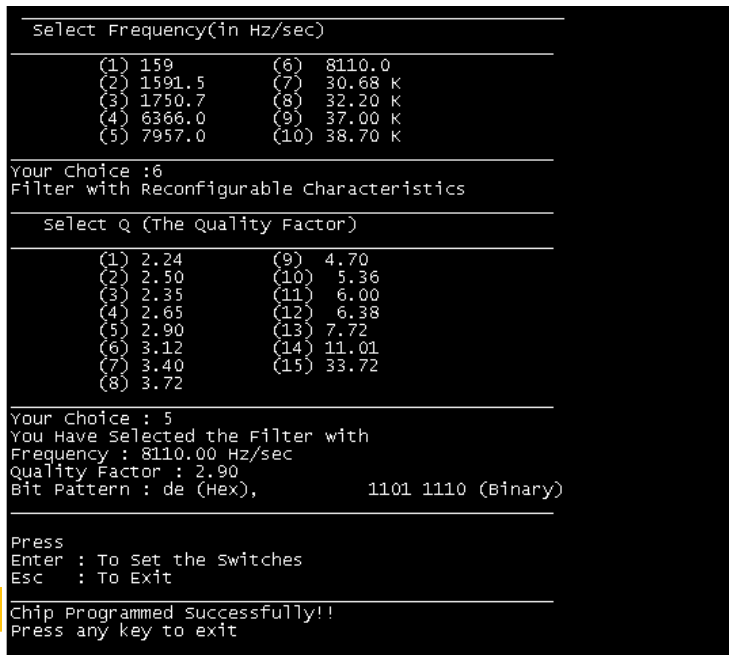

**Figure 2**

This user-friendly screen helps you configure the desired filter.

**Figure 1**

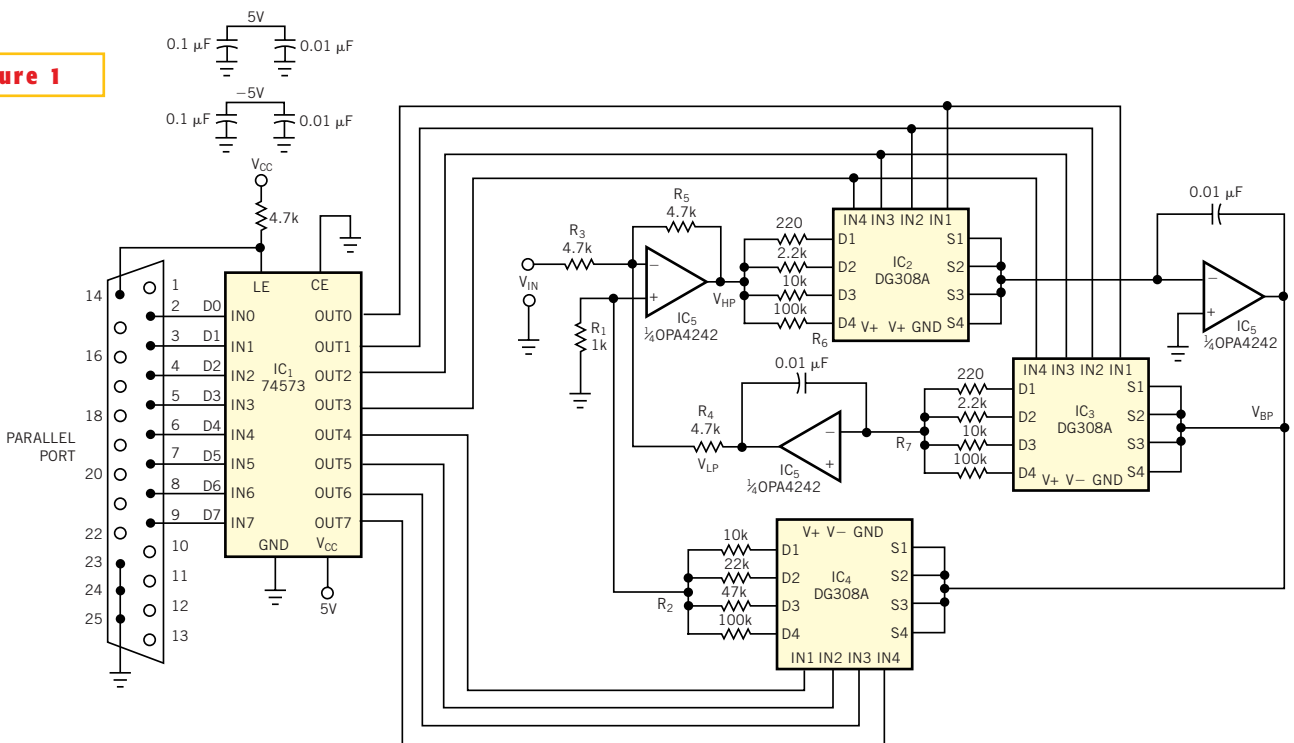

You can use a PC-configurable filter design to select both Q and center frequency.

based on a two-integrator configuration, provides simultaneous highpass, lowpass, and bandpass outputs.

By running simple code on the PC, you can choose from more than 150 programmable combinations of Q factor and center frequency (Listing 1). You can thus build a filter of desired parameters on the fly. The design uses quad analog switches DG308 from Maxim (www.maxim-ic.com) together with octal latches for programmability. A micropower precision op amp, OPA4242, from Burr-Brown (www.ti.com) makes up the ana-

**TABLE 1—DATA BITS FOR Q SELECTION**

D9 (100k)	D8 (47k)	D7 (22k)	D6 (j10k)	Q
1	1	1	1	2.24
0	1	1	1	2.35
1	0	1	1	2.5
0	0	1	1	2.65
1	1	0	1	2.9
0	1	0	1	3.12
1	0	0	1	3.4
0	0	0	1	3.72
1	1	1	0	4.7
0	1	1	0	5.36
0	1	0	0	6
1	0	1	0	6.38
0	0	1	0	7.72
1	1	0	0	11.01
1	0	0	0	33.72

log-filter section. The software provides the data bits on ports pin 2 through 9, stored in the latch that controls the analog switches and, hence, selects the appropriate resistance combination to select the desired Q and  $f_0$  values. The center frequency and Q values are:  $f_0 = [1/C_1 C_2 R_{p6} R_{p7}]^{1/2}$  and  $Q = (1 + R_{p2}/R_1)/3$ , where  $R_{p2}$ ,  $R_{p6}$ , and  $R_{p7}$  are PC-programmable resistances.

Data nibbles from port pins D2 through D5 provide ganged-switch settings for  $R_{p6}$  and  $R_{p7}$ , ensuring that they are always equal. Data nibbles correspon-

**LISTING 1—C PROGRAM FOR PC-CONFIGURABLE FILTER**

```
#include <dos.h>
#include <conio.h>
#include <stdio.h>
#include <process.h>
#define LPT 0x378 /* Data Port Address */
#define COM1 0x37A /* Control Port Address */
#define ESC 0x1B
typedef unsigned char u08;
enum boolean {false,true};

/* Function Declarations */
void chip_program(u08); /* To set the analog switches */
void showbits(u08); /* To see bit pattern */
void Dr_line(void); /* Draw a line */
void init(void); /* Initializes the Parallel Port */

void main()
{
    int fch,ctr,qch;
    u08 pdat,todat;
    float freq,qqty;
    init();
    do{
        clrscr();
        printf("RECONFIGURABLE UNIVERSAL FILTER by saurav gupta & tejinder singh\n");
        Dr_line();
        printf("Select frequency(1n Hz/sec)\n");
        Dr_line();
        printf("\t(1) 159 \t(6) 8110.0\n");
        printf("\t(2) 1591.5\t(7) 30.68 k\n");
        printf("\t(3) 1750.7\t(8) 32.20 k\n");
        printf("\t(4) 6366.0\t(9) 37.00 k\n");
        printf("\t(5) 7957.0\t(10) 38.70 k\n");
        Dr_line();
        printf("your choice :");
        scanf("%d",&fch);
    }while(fch<1 || fch>10); /* loop until a valid choice is entered*/

    switch(fch)
    {
        case 1 : freq=159; pdat=0x08; break;
        case 2 : freq=1591.5; pdat=0x04; break;
        case 3 : freq=1750.7; pdat=0x0C; break;
        case 4 : freq=6366; pdat=0x02; break;
        case 5 : freq=7957; pdat=0x06; break;
        case 6 : freq=8110; pdat=0x0e; break;
        case 7 : freq=30680; pdat=0x01; break;
        case 8 : freq=32200; pdat=0x05; break;
        case 9 : freq=37000; pdat=0x03; break;
        case 10 : freq=38000; pdat=0x0F; break;
    }

    do{
        clrscr();
        printf("Filter with Reconfigurable characteristics\n");
        Dr_line();
        printf("Select Q (The Quality Factor)\n");
        Dr_line();
        printf("\t(1) 2.24\t(9) 4.70\n");
        printf("\t(2) 2.50\t(10) 5.36\n");
        printf("\t(3) 2.35\t(11) 6.00\n");
        printf("\t(4) 2.65\t(12) 6.38\n");
        printf("\t(5) 2.90\t(13) 7.72\n");
        printf("\t(6) 3.12\t(14) 11.01\n");
        printf("\t(7) 3.40\t(15) 33.72\n");
        printf("\t(8) 3.72\n");
        Dr_line();
        printf("your choice :");
        scanf("%d",&qch);
    }while(qch<1 || qch>15);
    switch(qch)
    {
        case 1 : qqty=2.24; tdat=0xF0; break;
        case 2 : qqty=2.50; tdat=0x80; break;
        case 3 : qqty=2.35; tdat=0x30; break;
        case 4 : qqty=2.65; tdat=0x00; break;
        case 5 : qqty=2.90; tdat=0x50; break;
        case 6 : qqty=3.12; tdat=0x10; break;
        case 7 : qqty=3.40; tdat=0x90; break;
        case 8 : qqty=3.72; tdat=0x70; break;
        case 9 : qqty=4.70; tdat=0xF0; break;
        case 10 : qqty=5.36; tdat=0x60; break;
        case 11 : qqty=6.00; tdat=0x40; break;
        case 12 : qqty=6.38; tdat=0xA0; break;
        case 13 : qqty=7.72; tdat=0x20; break;
        case 14 : qqty=11.01; tdat=0xC0; break;
        case 15 : qqty=33.72; tdat=0x80; break;
    }

    pdat=pdat|tdat;
    printf("\nyou have selected the filter with\n");
    printf("Frequency : %6.2f Hz/sec\nquality factor : %3.2f\n",freq,qqty);
    printf("Bit Pattern : ");
    showbits(pdat);
    printf("\n");
    Dr_line();
    printf("\nPress \nEnter : To Set the switches\NESC : To Exit");
    if(getch()==ESC)
        exit(0);
    chip_program(pdat);
    printf("\n");
    Dr_line();
    printf("Chip programmed Successfully!!\nPress any key to exit");
    getch();
}

void Dr_line(void)
{
    int ctr;
    for(ctr=0;ctr<50;ctr++)
        printf("%c",205);
    printf("\n");
}

void init(void)
{
    outport(COM1,0xFF);
    delay(100);
    outport(LPT,0x00);
    delay(100);
}

void chip_program(u08 pdat)
{
    outport(COM1,0x00);
    delay(200);
    outport(LPT,pdat);
    delay(200);
    outport(COM1,0xFF);
    delay(200);
}

void showbits(u08 num)
{
    int i,k,mask;
    printf("%x (hex)\t\t",num);
    for(i=7;i>=0;i--)
    {
        if(i==7 || i==6 || i==11)
            printf(" ");
        mask=0x0001<<i;
        k=num & mask;
        k==0 ? printf("0"):printf("1");
    }
    printf(" (binary)");
}
C_code.txt
```

ding to pins D6 through D9 control the value of  $R_{p2}$ ; hence, you use them for Q-value selection. For the given resistance values, **Table 1** shows the data bits for different values of Q (ranging from 2.24 to 33.72). **Table 2** shows the data bits for various center frequencies (159 Hz to 38.70 kHz). **Figure 2** shows the software front-end screen to make the selection. The design uses an 8.11-kHz filter with Q-factor 2.9 for demonstration and hardware validation.

**Listing 1** gives the necessary back-end C code. The switches employed have a finite on-resistance,  $R_{DS}$ , of approxi-

**TABLE 2—DATA BITS FOR CENTER-FREQUENCY SELECTION**

D5	D4	D3	D2	f <sub>0</sub> (kHz)
1	0	0	0	0.159
0	1	0	0	1.519
1	1	0	0	1.75
0	0	1	0	6.37
0	1	1	0	7.96
1	1	1	0	8.11
0	0	0	1	30.68
0	1	0	1	32.2
0	0	1	1	37
1	1	1	1	38.7

mately 150Ω, which the design takes into account. For higher precision, you can

use better switches having on-resistances of approximately 35Ω. Note that more switches provide a wider range from which to select. You can choose the resistances to suit the application's bandwidth range. You can download the filter software from the Web version of this Design Idea at [www.edn.com](http://www.edn.com).

**Is this the best Design Idea in this issue?** Select at [www.edn.com](http://www.edn.com).

## Frequency source feeds entire lab

Mitchell Lee, Linear Technology Corp, Milpitas, CA


**P**LUMBING A LABORATORY with a standard frequency makes a lot of sense if the lab uses multiple frequency counters, spectrum analyzers, and other frequency-dependent test equipment. Rather than spending time keeping all of the instruments' oscillators in calibration or buying expensive, high-precision oscillators, you can use the circuit in **Figure 1** to distribute a single calibrated frequency source to the external-reference input of each instrument. The circuit represents a simple, 10-MHz source and distribution amplifier. The output comes not from the emitter or collector of the Colpitts-oscillator transistor,  $Q_1$ , but rather from the current flowing in the 10-MHz crystal. The common-base stage,  $Q_2$ , converts this current into a voltage and establishes the correct dc level for the output amplifier,  $IC_1$ . This IC contains four gain-of-two buffers with 110-MHz, 3-dB bandwidth and can drive

double-terminated 50 or 75Ω loads.

As **Figure 1** shows, the outputs use 75Ω impedance levels to take advantage of inexpensive F-type connector hardware and low-cost video coaxial cable.  $IC_1$  also provides good isolation between its outputs, so that changes in loading on one output do not affect the other outputs. The circuit delivers more than 6 dBm to each termination. If high accuracy and low drift are critical needs, you can substitute Hewlett-Packard's ([www.](http://www.hp.com)

[www.hp.com](http://www.hp.com)) HP10811A component oscillator for the Colpitts oscillator. Connect the HP10811A's output through a 510Ω resistor and a 10-nF coupling capacitor, directly to the emitter of  $Q_2$ . If you need more than four outputs, you can duplicate the  $IC_1$  stage as many times as necessary.

**Is this the best Design Idea in this issue?** Select at [www.edn.com](http://www.edn.com).

 

**Figure 1**

**A laboratorywide distribution system is an alternative to multiple frequency sources.**


# Circuit sequences supplies for FPGAs

David Daniels, Texas Instruments, Dallas, TX

**S**YSTEM DESIGNERS MUST consider the timing and voltage differences between core and I/O power supplies (in other words, power-supply sequencing) during power-up and power-down. The


possibility of a latch-up failure or excessive current draw exists when power-supply sequencing does not occur properly. The trigger for latch-up may occur if power supplies apply different potentials to the

core and the I/O interfaces. FPGAs and other components with different sequencing requirements further complicate the power-system design. To eliminate the sequencing problem, you should min-

 


**Figure 1**

This power-supply-sequencing circuit eliminates latch-up problems and reduces FPGA start-up transient currents.

 

**Figure 2**

When the I/O-supply voltage decays, the core voltage gracefully follows suit.

 

**Figure 3**

As the I/O-supply voltage rises smoothly toward 3.3V, the core voltage clamps cleanly at 1.8V.

imize the voltage difference between the core and the I/O supplies during power-up and -down. The power supply in **Figure 1** regulates the 3.3V input voltage to the 1.8V core voltage and tracks the 3.3V I/O during power-up and -down to minimize the voltage differences between the supply rails.

The circuit in **Figure 1** comprises IC<sub>1</sub> and IC<sub>2</sub>, a TPS2034 power switch and a TPS54680 step-down switching regulator, respectively. Component IC<sub>1</sub> is a high-side power switch that generates a slow ramp that IC<sub>2</sub> tracks during start-up. The ramp time of 6 msec minimizes the inrush currents to the bulk capacitors on the power-switch and supply outputs. The slow ramp minimizes the transient-current draw of the FPGA. The power switch ensures that the I/O voltage is not applied to the load before IC<sub>2</sub> has enough bias voltage to operate and generate the core voltage. Assuming that the input supply voltage is at 3.3V on J<sub>1</sub>, floating the J<sub>2</sub> connector en-

ables component IC<sub>1</sub>. The I/O supply voltage, J<sub>3</sub>, slowly rises until it reaches 3.3V. As the I/O voltage rises, the core voltage supply, J<sub>4</sub>, rises accordingly until the voltage reaches 1.8V (**Figure 2**). The TPS54680 device incorporates an analog multiplexer on the TRACKIN pin to implement the tracking function.

During power-up and -down, when the voltage on the TRACKIN pin is lower than the internal reference of 0.891V, the voltage on the TRACKIN pin connects to the noninverting node of the error amplifier. When the TRACKIN pin is below 0.891V, the pin effectively functions as the switching regulator's reference. The resistor divider of R<sub>3</sub> and R<sub>4</sub> on the TRACKIN pin must equal the resistor divider of R<sub>1</sub> and R<sub>2</sub> in the feedback compensation to track with minimal voltage difference during power-up and -down. The TPS2034 has an on-resistance of 37 mΩ and can supply as much as 2A output current. The TPS54680 is a synchronous buck regula-

tor that contains two 30-mΩ MOSFETs. Because the TPS54680 can source and sink as much as 6A load current at efficiencies greater than 90%, the output can track another power-supply rail during power-down. When the IC<sub>1</sub> device becomes disabled by shorting J<sub>2</sub> to ground, the I/O supply voltage decays, and the core supply voltage follows once the I/O voltage falls below the core voltage (**Figure 3**). Typically, Schottky diodes connect to the output of a dual power supply to clamp the voltage difference between the core and the I/O supplies during power-down, but most applications do not require the diodes with the power-supply circuit in **Figure 1**. Using this power-supply design reduces component count and increases reliability by eliminating the potential for latch-up and reducing FPGA start-up transient currents.

**Is this the best Design Idea in this issue?** Select at [www.edn.com](http://www.edn.com).